

Power Dividers and Hybrid Couplers

Name: Sparsh Arya

Registration Number: 17BEC0656

Slot: F1

Subject: Microwave Engineering

OBJECTIVE

For a given load of $Z_L = 28.3 - j44.2$,

1. For the given operating frequency and characteristic impedance, design power dividers and hybrid couplers with following design parameters.
2. Implement on standard substrate $\epsilon_r = 4.4$, $H = 1.6$ mm, $T = 0.05$ mm, $\tan\delta = 0.001$.
3. Compare the performance based on return loss, bandwidth, and quality factor for both solutions.
4. System Impedance (Ohm) = 30
5. Design Frequency (GHz) = 4.5
6. Parameters = $K^2 = 2/6$
7. All parts should be matched: $S_{ii} = 0$ or < -40 dB (practically)
8. Large isolation between output ports: $P(2,3) \Rightarrow S_{23} = S_{32}$
9. Reciprocal $S_{ij} = S_{ji}$ | where i is not equal to j
10. Loss-less condition: $|S_{11}|^2 + |S_{21}|^2 + |S_{31}|^2 = 1$
11. Power split: $K = 0.577 = P_3/P_2 = (S_{31})^2 / (S_{21})^2$

Procedure

Power Divider

1. Find the values of Z_{03} , Z_{02} , R , R_2 , R_3 .
2. Draw the schematic for the following circuit.
3. Run a frequency analysis for S parameters.
4. Tabulate the values.
5. Find the Bandwidth, Quality Factor and the return loss.

Hybrid Coupler

1. Find the values of Z_0 and $Z_0/(2)^{0.5}$.
2. Draw the schematic for the following circuit.
3. Run a frequency analysis for S parameters.
4. Tabulate the values.
5. Find the Bandwidth, Quality Factor and the return loss.

Calculations

Wilkinson Power divider

Design:

Given: $\epsilon_r = 4.4$
 $H = 1.6 \text{ mm}$
 $T = 0.05 \text{ mm}$
 $\tan \delta = 0.001$
 $f = 4.5 \text{ GHz}$
 $k^2 = 2/6 \text{ or } 1/3$

Thus, Power split ratio: $P_{1/2} = k^2 = 1/3$ ($\therefore k = 0.577$)

Calculations:

$Z_0(\text{given}) = 50 \Omega$
 $Z_{01} = Z_0 \sqrt{1 + k^2/k^2} = 79.024 \Omega$
 $Z_{02} = Z_{01} k^2 = 26.341 \Omega$
 $R = Z_0 (k + 1/k) = 69.303 \Omega$
 $R_2 = Z_0 k = 17.310 \Omega$
 $R_3 = Z_0/k = 51.993 \Omega$

Frequency range $\rightarrow f/2$ to $1.5f$
 2.25 GHz to 6.75 GHz

W and L for port 1: $W = 6.60607 \text{ mm}$
 $L = 8.69264 \text{ mm}$

port 2: $W = 7.88122 \text{ mm}$
 $L = 8.56113 \text{ mm}$

port 3: $W = 1.22905 \text{ mm}$
 $L = 9.37905 \text{ mm}$

Hybrid Coupler


Design:

$Z_0 = 30 \Omega$
 $Z_{0/2} = 30/6 = 21.216 \Omega$

$Z_0 \Rightarrow W = 6.60578$
 $L = 8.69268$


$Z_0/52 \Rightarrow W = 10.4416$
 $L = 8.49068$

Design

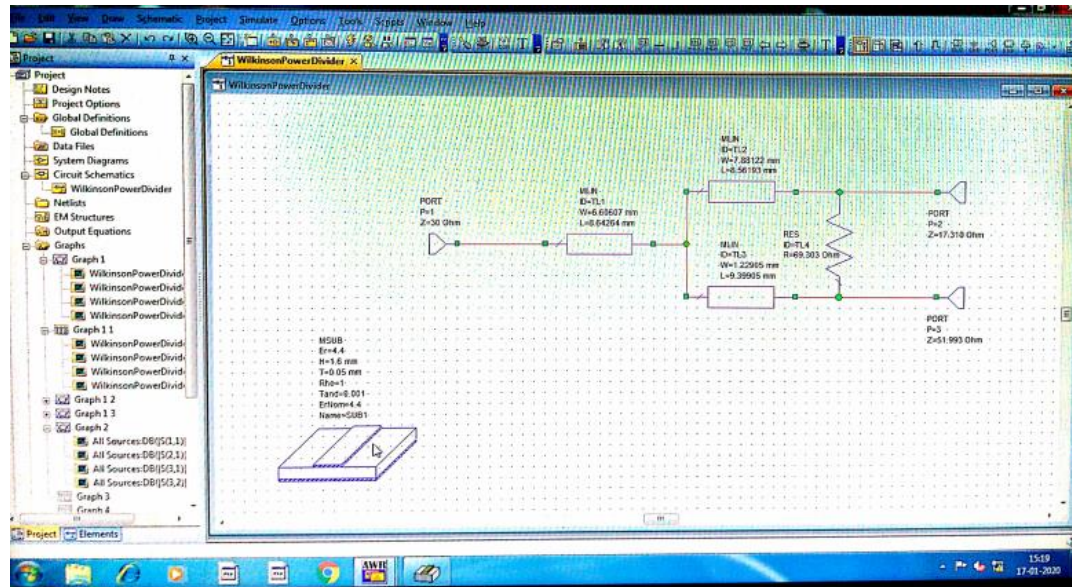



Wilkinson Power divider

Hybrid Coupler


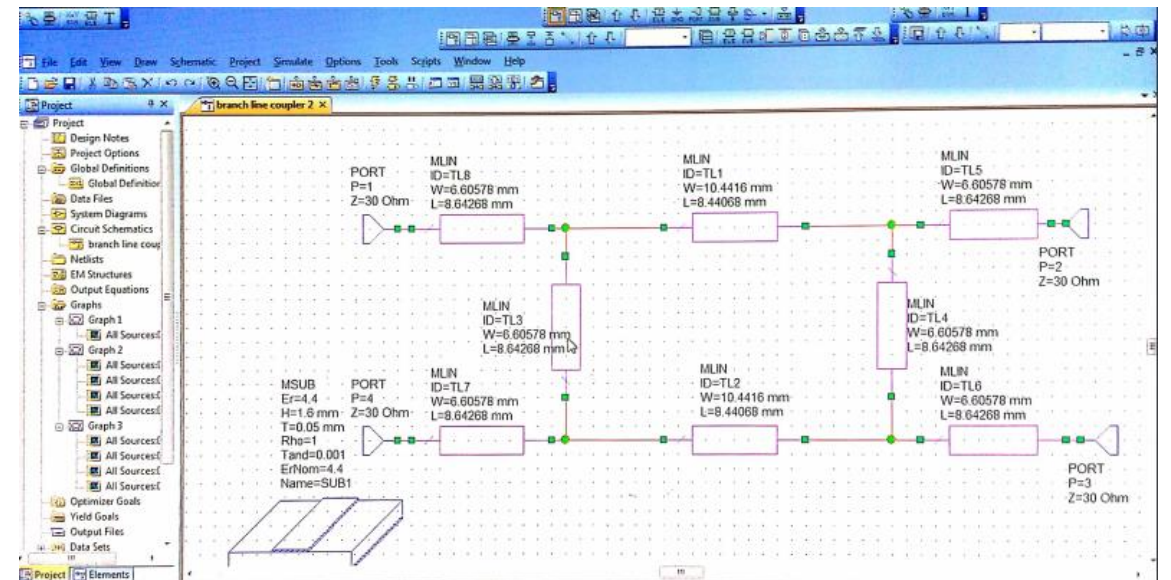


Graph

Wilkinson Power divider

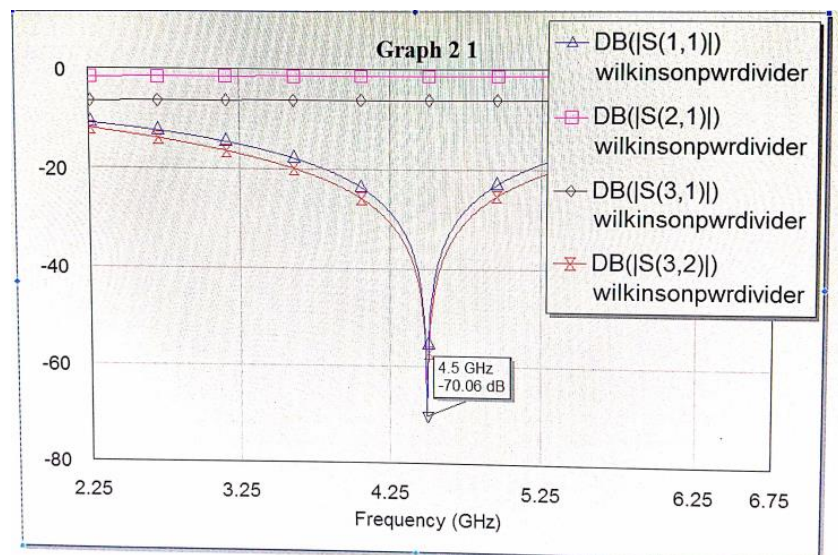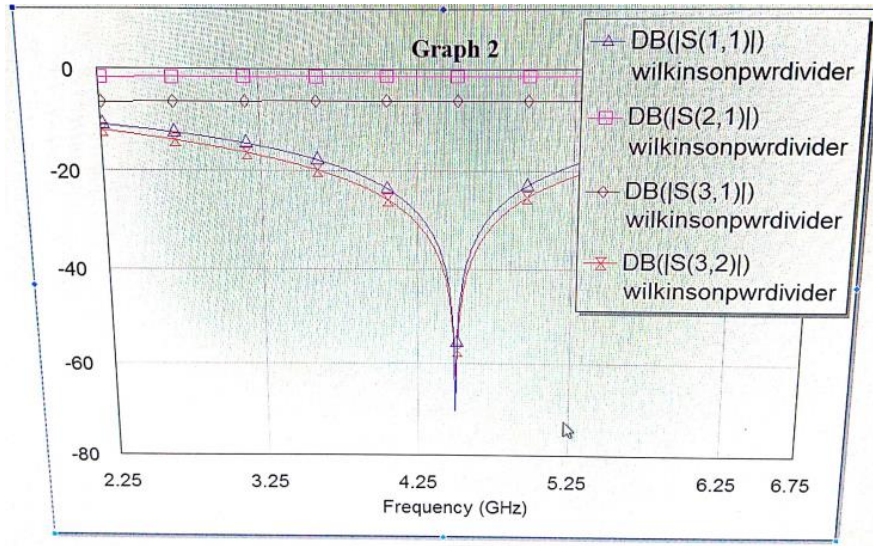

Hybrid Coupler

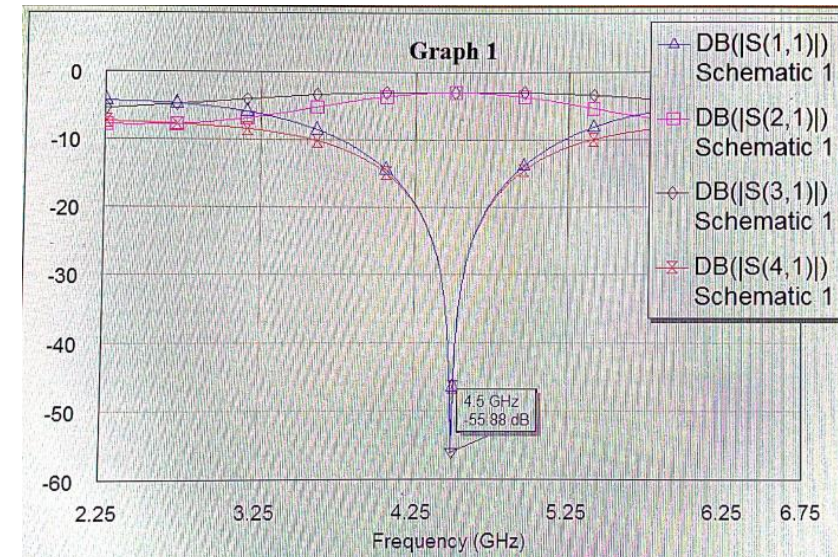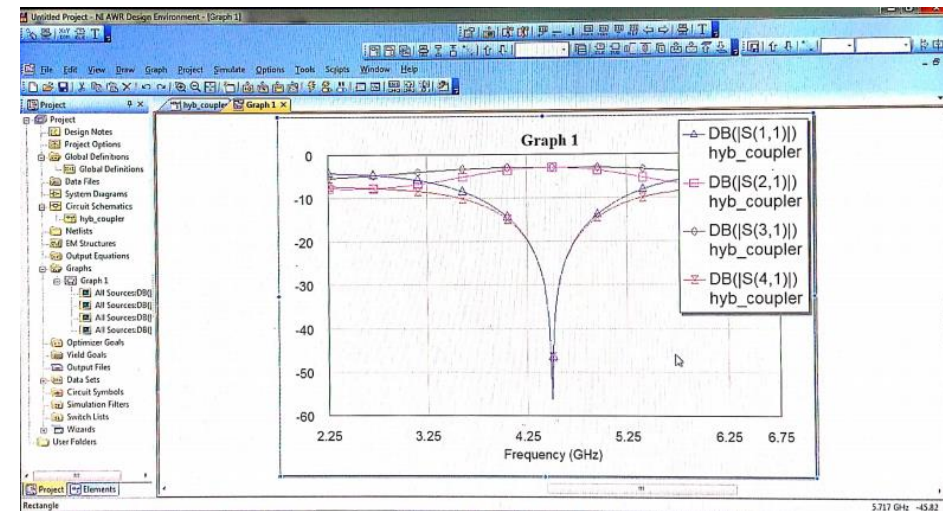

Tabular Readings

Wilkinson Power divider

Frequency (GHz)	DB(S(1,1)) wilkinsonpwrdivd	DB(S(2,1)) wilkinsonpwrdivd	DB(S(3,1)) wilkinsonpwrdivd	DB(S(3,2)) wilkinsonpwrdivd
4.47	-46.936	-1.2743	-6.0468	-48.86
4.48	-50.529	-1.2743	-6.0467	-52.145
4.49	-56.715	-1.2743	-6.0467	-57.107
4.5	-70.256	-1.2744	-6.0467	-62.7
4.51	-55.602	-1.2744	-6.0467	-57.265
4.52	-49.95	-1.2745	-6.0467	-52.24
4.53	-46.538	-1.2747	-6.0467	-48.922
4.54	-44.091	-1.2748	-6.0468	-46.493
4.55	-42.182	-1.2749	-6.0468	-44.585
4.56	-40.616	-1.2751	-6.0469	-43.017
4.57	-39.289	-1.2753	-6.0471	-41.686
4.58	-38.138	-1.2755	-6.0472	-40.531
4.59	-37.121	-1.2758	-6.0474	-39.51
4.6	-36.21	-1.276	-6.0476	-38.596
4.61	-35.385	-1.2763	-6.0478	-37.769
4.62	-34.632	-1.2766	-6.048	-37.013
4.63	-33.938	-1.2769	-6.0482	-36.318
4.64	-33.296	-1.2773	-6.0485	-35.673
4.65	-32.697	-1.2776	-6.0488	-35.073
4.66	-32.137	-1.278	-6.0491	-34.512
4.67	-31.611	-1.2784	-6.0495	-33.984
4.68	-31.114	-1.2788	-6.0498	-33.487
4.69	-30.645	-1.2793	-6.0502	-33.016
4.7	-30.199	-1.2797	-6.0506	-32.569
4.71	-29.775	-1.2802	-6.051	-32.145

Hybrid Coupler

Frequency (GHz)	DB(S(1,1)) hyb_coupler	DB(S(2,1)) hyb_coupler	DB(S(3,1)) hyb_coupler	DB(S(4,1)) hyb_coupler
4.35	-23.829	-3.1327	-3.0611	-23.919
4.36	-24.43	-3.1236	-3.061	-24.511
4.37	-25.076	-3.1152	-3.0609	-25.148
4.38	-25.774	-3.1074	-3.0609	-25.837
4.39	-26.532	-3.1002	-3.0608	-26.587
4.4	-27.362	-3.0936	-3.0608	-27.41
4.41	-28.279	-3.0877	-3.0608	-28.321
4.42	-29.305	-3.0824	-3.0608	-29.339
4.43	-30.467	-3.0778	-3.0608	-30.495
4.44	-31.809	-3.0738	-3.0608	-31.83
4.45	-33.395	-3.0704	-3.0608	-33.409
4.46	-35.335	-3.0677	-3.0608	-35.34
4.47	-37.83	-3.0656	-3.0609	-37.82
4.48	-41.321	-3.0641	-3.0609	-41.282
4.49	-47.073	-3.0633	-3.0609	-46.92
4.5	-56.237	-3.0631	-3.061	-55.421
4.51	-46.56	-3.0636	-3.061	-46.55
4.52	-41.037	-3.0647	-3.0611	-41.073
4.53	-37.633	-3.0665	-3.0611	-37.675
4.54	-35.182	-3.0689	-3.0611	-35.226
4.55	-33.268	-3.072	-3.0612	-33.314
4.56	-31.699	-3.0757	-3.0612	-31.747
4.57	-30.368	-3.08	-3.0613	-30.42
4.58	-29.214	-3.085	-3.0614	-29.27
4.59	-28.194	-3.0907	-3.0615	-28.255
4.6	-27.28	-3.0969	-3.0616	-27.347
4.61	-26.453	-3.1039	-3.0617	-26.536

Results

- Bandwidth= 4.5
- Quality factor= $70.06/4.5=15.70$
- Return loss= 70.256 dB

Wilkinson Power divider

- Bandwidth= 4.5
- Quality factor= $55.88/4.5=12.41$
- Return loss= 56.237dB

Hybrid Coupler

Inferences

The Circuit diagram has been created for dividing input power in the ratio of 2:6 by designing a power divider and a hybrid coupler.

The graphs have been constructed and the output values such as return loss, bandwidth and quality factor has been recorded.

References

- Microwave Engineering- David M. Pozar
- https://www.tutorialspoint.com/microwave_engineering/microwave_engineering_introduction.htm
- <https://www.microwaves101.com/encyclopedias/waveguide-mathematics>
- [https://en.wikipedia.org › wiki › Microwave_engineering](https://en.wikipedia.org/wiki/Microwave_engineering)